

SECTION A

Answer ALL questions in this section.

1. (a) State the following laws as applied in D.C circuits:
- Ohm's law;
 - Kirchhoff's voltage law. (4 marks)
- (b) Show, with the aid of a circuit diagram, that the total resistance in a parallel circuit given by $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ (4 marks)
- (c) From the network shown in figure 1, use Kirchhoff's laws to determine the;
- branch currents;
 - power dissipated by 6Ω resistor;
 - energy consumed by 3Ω resistor after 15 seconds. (12 marks)

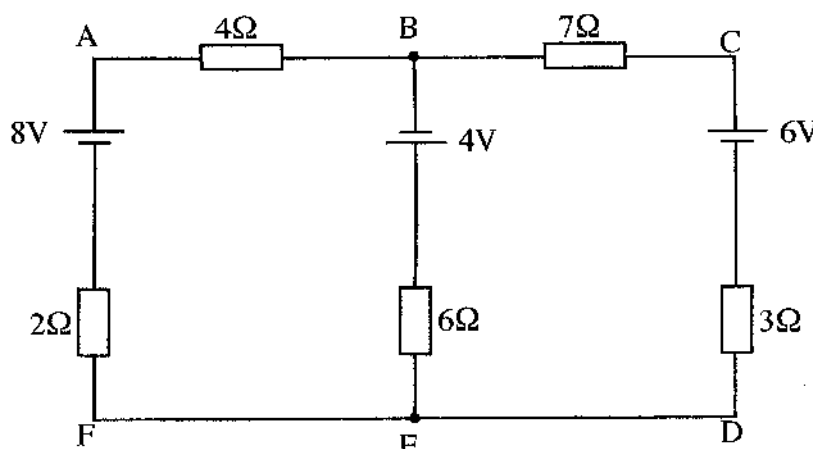


Figure 1

2. (a) Define the following terms as used in electrostatics.
- relative permittivity;
 - electric field strength. (4 marks)
- (b) An electrical circuit has two capacitors of $8\mu\text{F}$ and $14\mu\text{F}$ connected in parallel. Another capacitor of $16\mu\text{F}$ is in series with the parallel section. The series-parallel combination is connected across a terminal voltage of 240V. Determine the:
- total capacitance;
 - p.d. across each capacitor;
 - charge stored by each capacitor;
 - energy stored by $16\mu\text{F}$ capacitor. (10 marks)

- (c) The resistance of a copper coil is 300 Ohms at 20°C. The room temperature increases and the resistance of the coil rises to 375 Ohms. If the temperature coefficient of resistance of copper is 0.04°C at 20°C, determine the temperature to which the coil has risen. (6 marks)
3. (a) State **three** types of transistor configurations. (3 marks)
- (b) With the aid of energy band theory sketches, state the difference between the following terms:
 (i) insulators;
 (ii) conductors;
 (iii) semi-conductors. (6 marks)
- (c) With the aid of a diagram, explain the construction and operation of a photodiode. (5 marks)
- (d) Simply the following boolean equation by using a Karnaugh map.
 $F = \overline{A}BCD + \overline{A}BC\overline{D} + ABCD + BC\overline{D}$ (6 marks)
4. (a) (i) State the law of conservation of energy. (2 marks)
- (ii) Distinguish between:
 (a) Renewable and non-renewable energy.
 (b) Elastic and gravitational potential energy. (8 marks)
- (b) Explain how each of the following natural sources of energy are harvested to produce electrical energy.
 (i) sun
 (ii) wind
 (iii) high dam (3 marks)
- (c) A body of mass 3.5Kg is pulled from rest by a horizontal force of 10.5N for 3 seconds calculate.
 (i) the distance covered by the body.
 (ii) the Kinetic energy gained by the body (ignore friction). (7 marks)

SECTION B

Answer any **ONE** question from this section.

5. (a) Define the term transducer. (2 marks)
- (b) With the aid of a circuit diagram, explain the operation of a full-wave bridge rectifier. (7 marks)
- (c) State any **three** types of feedback connections as applied to amplifiers. (3 marks)
- (d) (i) Perform the following binary arithmetics.
- (I)
$$\begin{array}{r} 110 \\ + 011 \\ \hline \end{array}$$
 (II)
$$\begin{array}{r} 111 \\ \times 10 \\ \hline \end{array}$$
- (ii) Convert the following numbers as instructed.
- (I) 431_{10} to excess 3 code. (8 marks)
- (II) 11011_2 to gray code.

6. (a) Draw the equivalent logic gates symbols for the symbols shown in figure 2 (a) and (b).

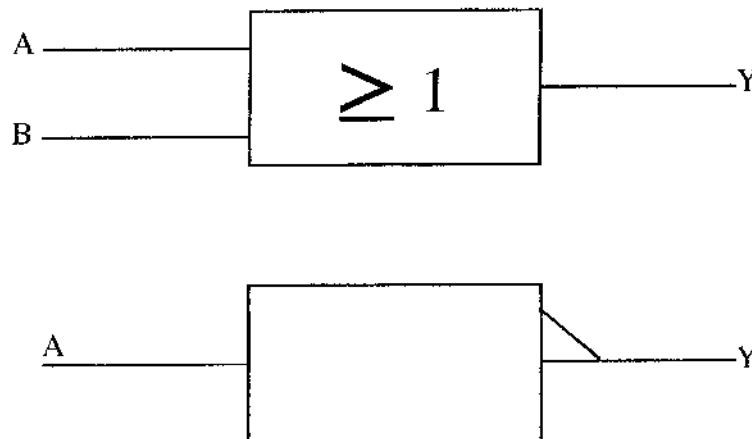


Figure 2

(2 marks)

- (b) Draw a logical circuit diagram of a SR flip-flop using NOR gates and explain its operation. (6 marks)
- (c) (i) Explain with the aid of a circuit diagram, the operation of an LC low pass filter. (6 marks)

(ii) From the circuit shown in figure 3, calculate:

- I. Base current.
- II. Collector current.
- III. Collector emitter voltage.

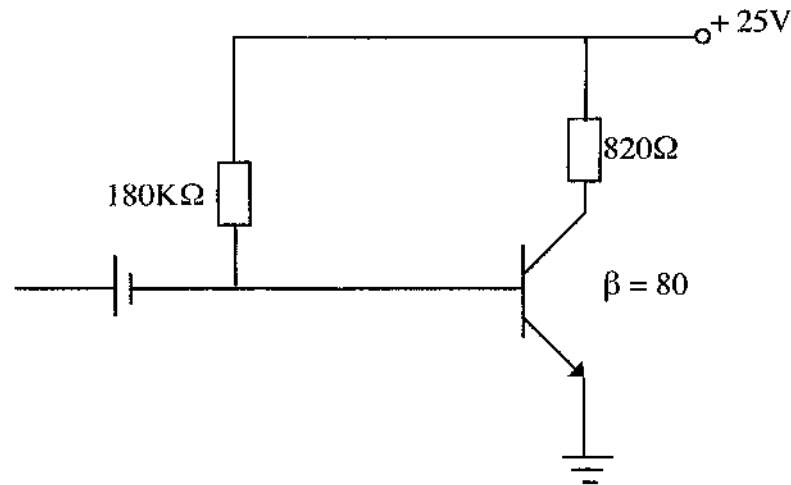


Figure 3

(6 marks)

7. (a) Define the following terms as used in magnetic circuits.

- (i) magnetomotive force.
- (ii) Reluctance.

(4 marks)

(b) A mild steel close magnetic circuit has a mean length of 50mm and a cross-sectional area of 420mm^2 . A current of 0.6A flows in a coil wound uniformly around the circuit, where the flux of $300\ \mu\text{Wb}$ is produced. If the relative permeability steel is 400, Calculate the:

- (i) Reluctance of the coil.
- (ii) Number of turns of the coil.
- (iii) Flux density.

(8 marks)

(c) A single phase transformer has 3000 turns on the primary side and 1200 turns on the secondary side. Its no-load current is 6A at a power factor of 0.25 lagging, while the secondary current is 90 A at a power factor of 0.88 lagging.

Determine the primary current and the power factor.

(8 marks)

8. (a) (i) State any **two** modes of heat transfer.
(ii) Define the term specific latent heat of vaporisation. (4 marks)
- (b) (i) Outline any **four** properties of electro-magnetic waves.
(ii) An X-ray machine produces radiation of wavelength $1.0 \times 10^{-11} \text{m}$. Calculate
I. the frequency of its radiation.
II. its energy content if the planks constant is equal to $6.63 \times 10^{-34} \text{Js}$ (8 marks)
- (c) The mass of a copper calorimeter and stirrer is 60g. It is filled with 100g of water at a room temperature of 25°C . Steam is passed until the temperature of the water reaches 45° . When the calorimeter is reweighed, its mass is 163.5g. Calculate the specific latent heat of vaporisation of water.
(Specific heat capacity of copper is $400 \text{J/kg}^\circ\text{C}$ and that of water is $4200 \text{J/kg}^\circ\text{C}$). (8 marks)