

## SECTION A

Answer any **THREE** questions from this section.

1. (a) State the following laws as applied to electrical circuits:
- Ohm's law;
  - Kirchhoff's voltage law.
- (4 marks)
- (b) A coil of copper wire has a resistance of  $80 \Omega$  at  $20^\circ\text{C}$ . If the temperature coefficient of resistance of copper at  $0^\circ\text{C}$  is  $0.0043/^\circ\text{C}$ , calculate the resistance of the coil at  $50^\circ\text{C}$ .
- (5 marks)
- (c) Figure 1 shows an electric circuit: Use Kirchhoff's laws to determine the:
- currents flowing through each resistor;
  - power dissipated by  $6 \Omega$  resistor;
  - energy consumed by  $5 \Omega$  resistor after 15 minutes.
- (11 marks)

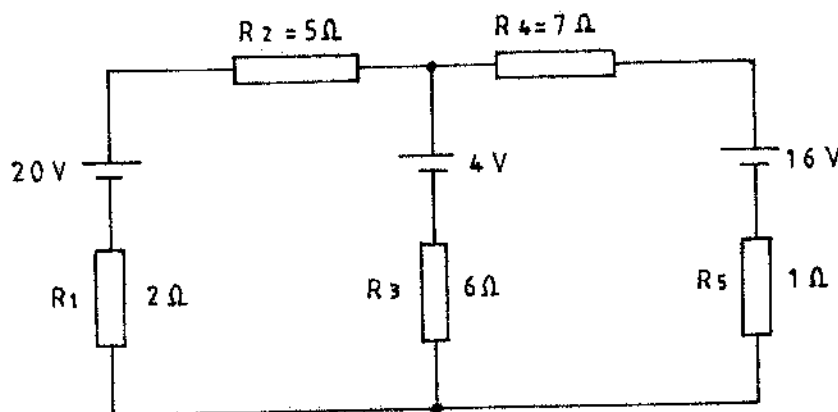


Fig. 1

2. (a) Define the following terms as used in electrostatics:
- capacitance;
  - electric field intensity.
- (4 marks)
- (b) With the aid of a labelled circuit diagram, derive the formular for the total capacitance of three capacitors connected in series.
- (6 marks)

(c) Figure 2 shows an electric circuit. Determine the:

- (i) total capacitance of the whole circuit;
- (ii) voltage drop across  $C_2$ ;
- (iii) energy stored by  $C_4$ ;
- (iv) electric flux stored by  $C_5$ .

(10 marks)

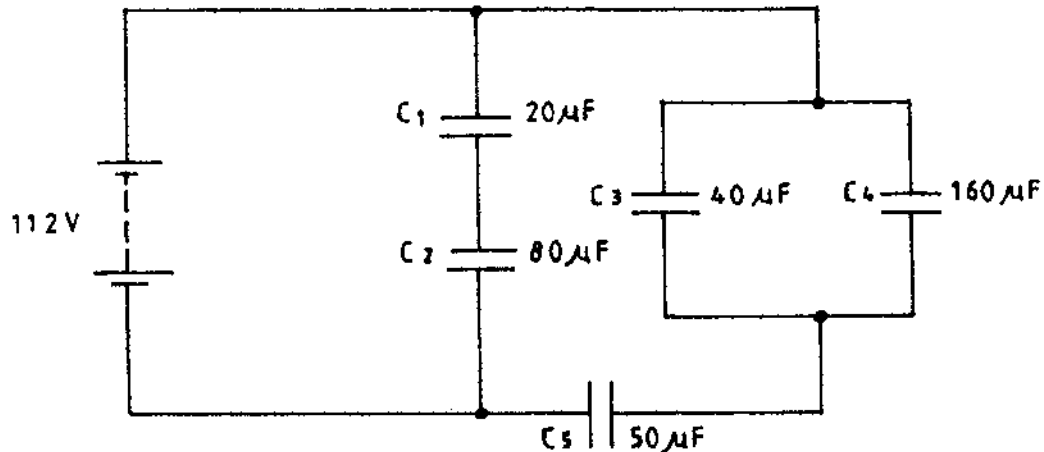


Fig. 2

3. (a)
- (i) State the inverse square law of electromagnetic waves.
  - (ii) Outline **five** properties of electromagnetic waves.
  - (iii) Calculate the wave length of a radio wave if the frequency is 2.5 mega Hertz and a velocity of  $3 \times 10^8$  m/s.

(10 marks)

(b) State:


- (i) the **two** laws of reflection;
- (ii) any **three** applications of curved mirrors.

(5 marks)

- (c)
- (i) The critical angle for water is  $48.5^\circ$ . Calculate its refractive index.
  - (ii) How many images would be seen from two mirrors whose reflection surface make an angle of  $12^\circ$  to each other?

(5 marks)

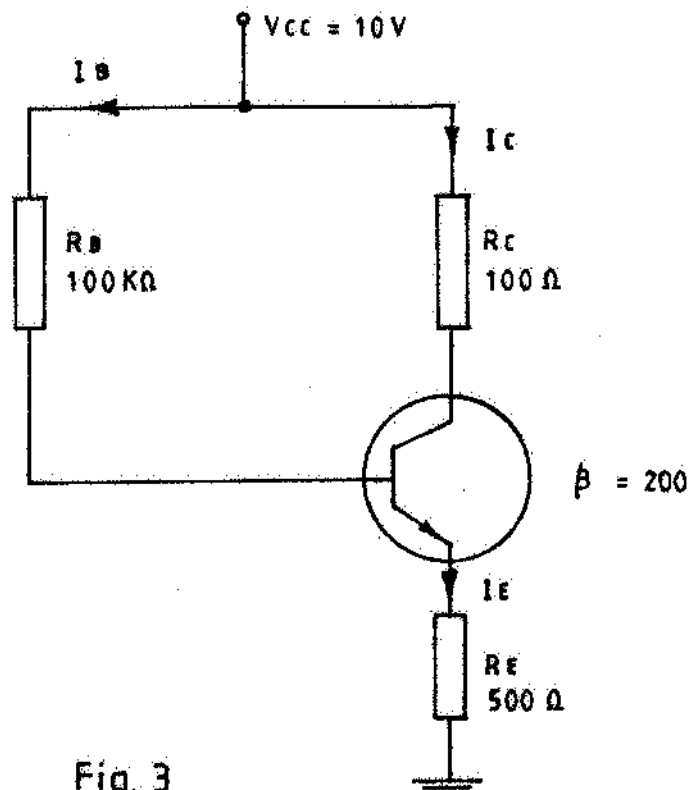4. (a) Explain the following terms as applied in semi-conductors:
- atomic structure;
  - valence.
- (4 marks)
- (b) State any two applications of the following components in electronics:
- silicon controlled rectifier (SCR);
  - light emitting diodes (LED).
- (4 marks)
- (c) Draw the output signals to differentiate the classes of amplifiers. (6 marks)
- (d) Figure 3 shows a transistor circuit. Neglecting the base-emitter voltage drop, determine the currents:
- $I_B$ ;
  - $I_C$ ;
  - $I_E$ .
- (6 marks)



## SECTION B

Answer any **TWO** questions from this section.

5. (a) Define the following terms:
- (i) magnetomotive force;
  - (ii) magnetic field intensity.
- (4 marks)
- (b) A circular ring has a cross-sectional area of  $40 \text{ mm}^2$  and a radius of  $30 \text{ mm}$ . A current of  $0.6 \text{ A}$  flows through the coil wound uniformly around the ring to produce a flux of  $0.2$  milli-webers. If the relative permeability of this value of current is  $400$ , find the:
- (i) reluctance of the mild steel ring;
  - (ii) number of turns of the coil;
  - (iii) flux density in the ring.
- (8 marks)
- (c) (i) Name any **three** types of transformers.
- (ii) A  $150 \text{ kVA}$  transformer has a full load copper loss of  $1.8 \text{ kW}$  and an iron loss of  $1.2 \text{ kW}$ . Determine the efficiency of the transformer at full load and  $0.88$  power factor.
- (8 marks)
6. (a) Define the following terms:
- (i) kinetic energy;
  - (ii) potential energy.
- (4 marks)
- (b) Determine the power of a water pump required to lift  $300 \text{ kg}$  of water through a vertical height of  $6 \text{ M}$  in nine seconds. (Assume  $g = 10 \text{ m/s}^2$ )
- (6 marks)
- (c) Define the:
- (i) specific latent heat of fusion;
  - (ii) specific heat capacity.
  - (iii) a block of  $50 \text{ g}$  of ice at  $0^\circ \text{C}$  is added to  $200 \text{ g}$  of water at  $70^\circ \text{C}$  in a vacuum flask. When all the ice has melted, the temperature falls to  $40^\circ \text{C}$ . Calculate the specific latent heat of fusion of ice neglecting any heat loss to the surrounding. (specific heat capacity of water =  $4200 \text{ J/kgK}$ )
- (10 marks)

7. (a) Draw a labelled block diagram of a regulated d.c. power supply. (3 marks)
- (b) Figure 4 shows a rectifier circuit. Determine:
- maximum value of load voltage;
  - peak value of load current;
  - power absorbed by the load.

(8 marks)

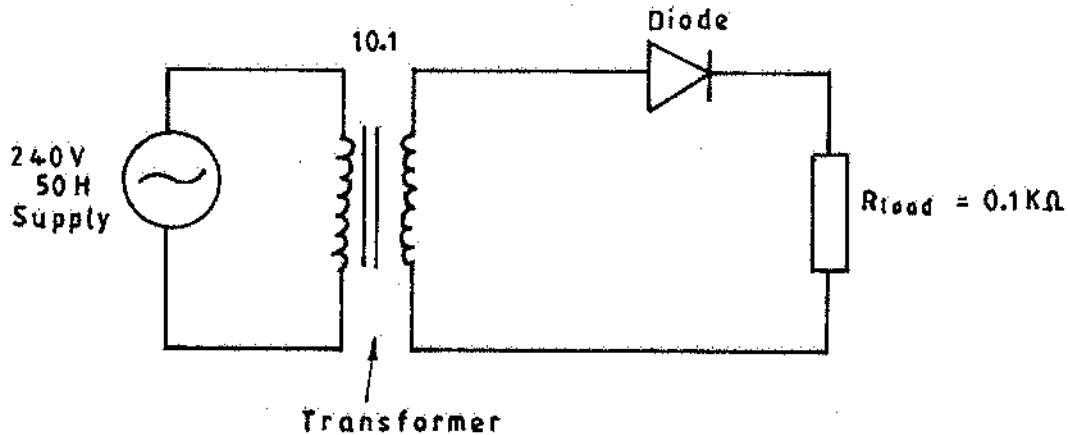


Fig. 4

- (c) (i) State **three** advantages of negative feedback in amplifiers.
- (ii) With aid of a diagram, derive the expression for closed loop gain of an amplifier with positive feedback.

(9 marks)

8. (a) Prove the following Boolean identity.

$$A + \overline{A}B = A + B$$

(5 marks)

(b) (i) State **three** applications of logic gates.

(ii) Figure 5 shows a two input OR logic gate. Write its truth table.

(7 marks)

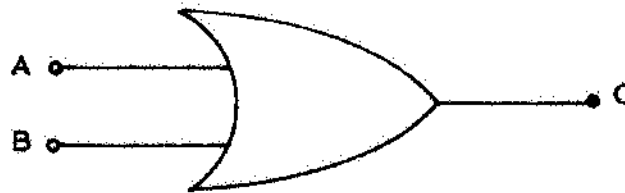


Fig. 5

(c) Multiply  $1101_2$  by  $1100_2$ .

(2 marks)

(d) With aid of a diagram, describe the principle of operation of a capacitive transducer.

(6 marks)

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---