

2521/204 2602/204
2601/204 2603/204
ENGINEERING DRAWING AND
CIRCUIT ANALYSIS
June/July 2020
Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING
(POWER OPTION)
(TELECOMMUNICATION OPTION)
(INSTRUMENTATION OPTION)

MODULE II

ENGINEERING DRAWING AND CIRCUIT ANALYSIS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Mathematical tables/Non-programmable scientific calculator;

Drawing instruments;

Drawing paper size A2;

Computer installed with Auto CAD, electronic CAD software and printer.

This paper consists of EIGHT questions in TWO sections; A and B.

Answer any THREE questions from section A and any TWO questions from section B in the answer booklet and drawing papers provided.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

All drawing dimensions are in mm.

Candidates should answer the questions in English.

This paper consists of 6 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

SECTION A: CIRCUIT ANALYSIS

Answer any **THREE** questions from this section.

1. (a) Define 'Harmonics' as used in complex waveforms. (1 mark)

- (b) A complex wave of r.m.s value 240 V has 22% third harmonic and 5% fifth harmonic content. Determine the r.m.s values of:

- (i) fundamental wave;
 (ii) third and fifth harmonics.

(7 marks)

- (c) (i) Describe a 'Two-Port Network'.
 (ii) List **three** examples of Two-Port networks.
 (iii) **Figure 1** represents a passive Two-Port network which gives rise to input impedance equal to load impedance Z_L . Show that the input impedance:

$$\frac{V_1}{I_1} = Z_i = [Z_1(Z_1 + 2Z_2)]^{\frac{1}{2}}$$

(12 marks)

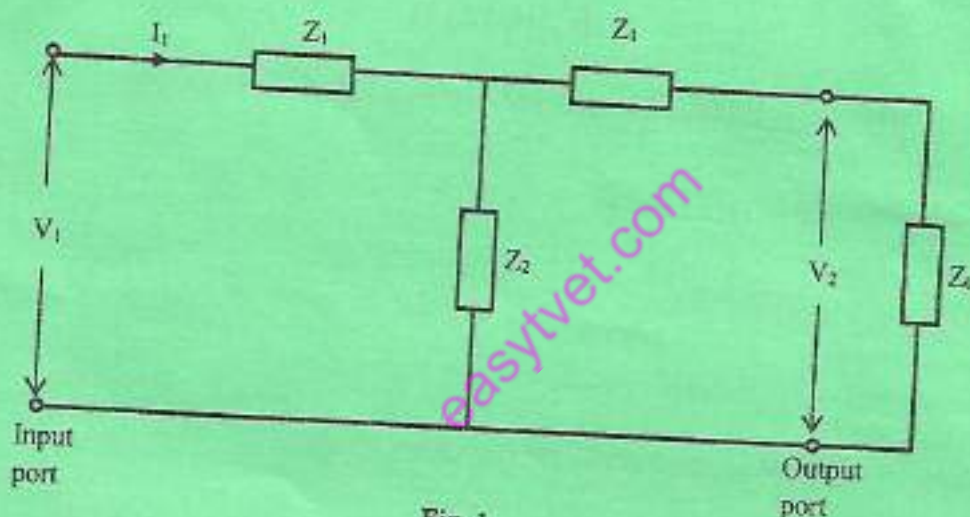


Fig. 1

2. (a) (i) State two advantages of three phase systems over single phase systems.
 (ii) Explain each of the following as used in three phase systems:

- I. phase sequence;
 II. double subscript notation V_{xy} .

(4 marks)

- (b) A balanced three-phase delta connected load has per phase impedance of $(25 + j40)\Omega$. If 400 V, three phase supply is connected to the load, determine the:

- (i) phase current;
 (ii) line current;
 (iii) power factor;
 (iv) power supplied to the load.

(8 marks)

- (c) (i) State **two** properties of an ideal transformer.
(ii) Explain the need for carrying out a short circuit test on a three phase transformer.
(iii) Draw the circuit diagram for the test in (c)(ii). (8 marks)
3. (a) (i) State **two** advantages of three phase induction motors.
(ii) Sketch the power flow stages for a three phase induction motor, indicating the power losses in each stage. (10 marks)
- (b) (i) Explain the need for a starter in a three phase induction motor.
(ii) List any **two** methods of starting a three phase induction motor. (4 marks)
- (c) (i) Sketch the equivalent circuit diagram of a capacitor start, capacitor run single phase induction motor.
(ii) List **two** types of single phase synchronous motors. (6 marks)
4. (a) (i) Explain the reason why a three phase synchronous motor is supplied with both A.C and D.C voltages.
(ii) A 1200 kW load at 0.6 p.f lagging is connected across a three phase synchronous motor. If the power factor of the load is improved to unity, determine the kVAR rating of the motor. (6 marks)
- (b) (i) Draw a labelled diagram of the pony motor method of starting a three phase synchronous motor.
(ii) State **two** applications of the motor in (b)(i). (7 marks)
- (c) **Figure 2** shows a series R-C circuit. Derive an expression for the supply voltage E at any time during charging of the capacitor. (7 marks)

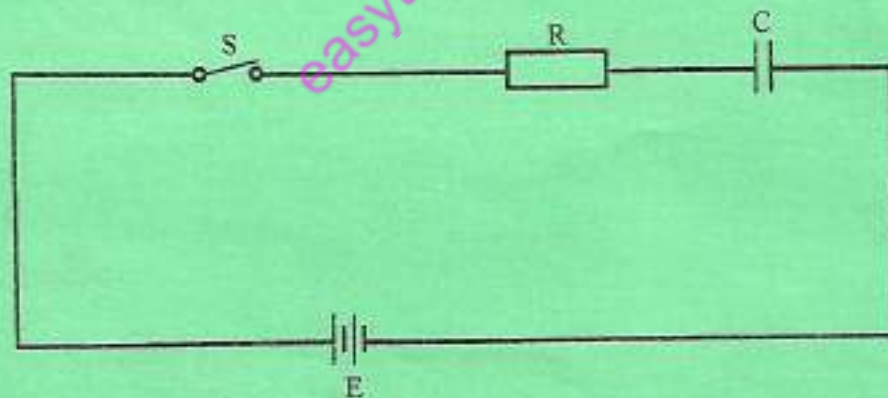


Fig. 2

5. (a) (i) Distinguish between an amplidyne and a metadyne machine.
(ii) Explain the function of each of the following parts of a d.c motor:
- I. stator poles;
II. rotor. (4 marks)

- (b) (i) State **two** effects of armature reaction in d.c generators.
 (ii) With the aid of diagrams, explain the process of commutation in d.c generators. (8 marks)
- (c) (i) Draw a labelled diagram of a three point starter for a d.c shunt motor.
 (ii) State **two** applications of d.c compound motors. (8 marks)

SECTION B: ENGINEERING DRAWING

Answer any **TWO** questions from this section.

6. (a) Construct a regular pentagon in a circle of diameter 120 mm. (6 marks)
- (b) **Figure 3** shows three points A, B and C.



Fig. 3

Construct a circle to pass through the three given points.

(6 marks)

- (c) **Figure 4** shows two circles blending with an arc.

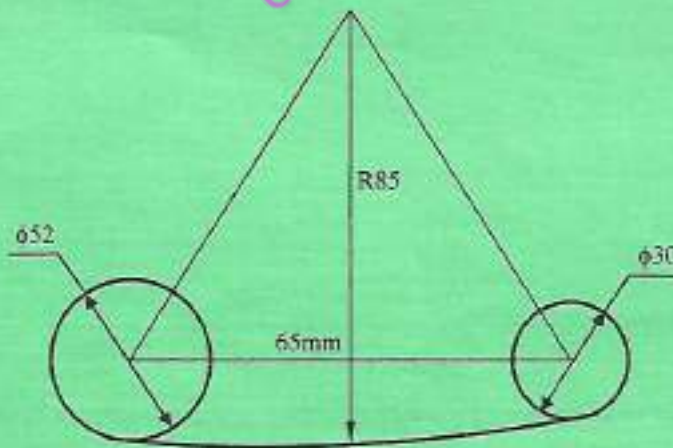


Fig. 4

Draw the profile clearly showing the centre of the arc.

(8 marks)

7. (a) Draw a ladder diagram for a forward-reverse three phase motor starter. (10 marks)

(b) Sketch the following BS3939 symbols:

- (i) switched socket outlet;
- (ii) one gang two way switch;
- (iii) push button;
- (iv) motor;
- (v) inductor.

(5 marks)

(c) Figure 5 shows a bell circuit.

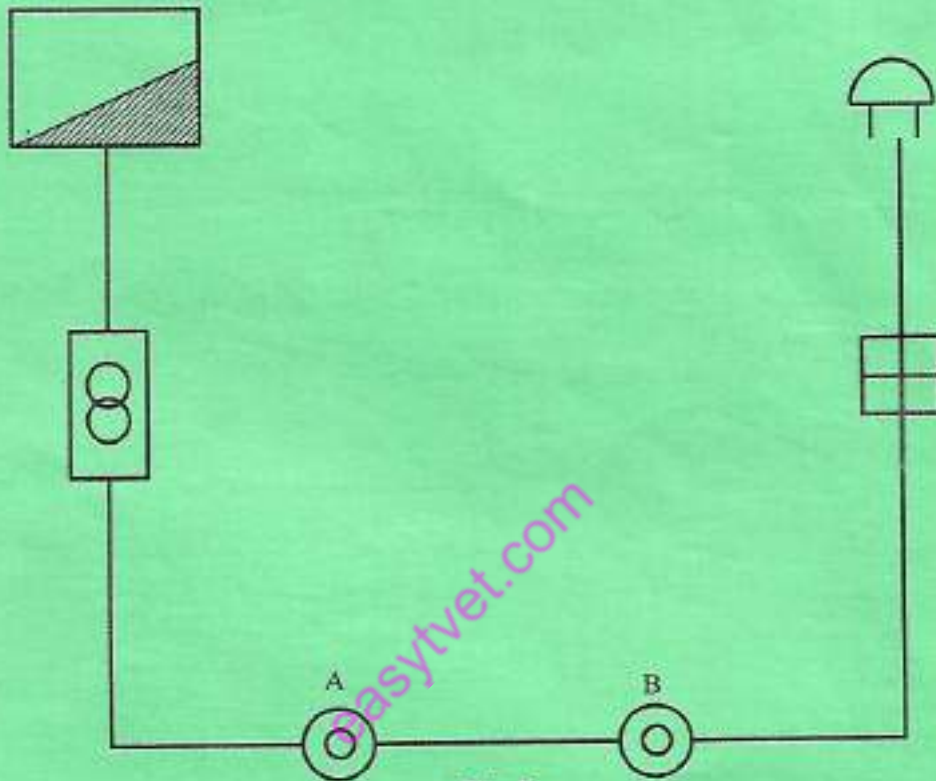


Fig. 5

Draw the wiring diagram such that push buttons A and B controls the bell independently via a relay. (5 marks)

8. (a) Figure 6 shows an electronics circuit.

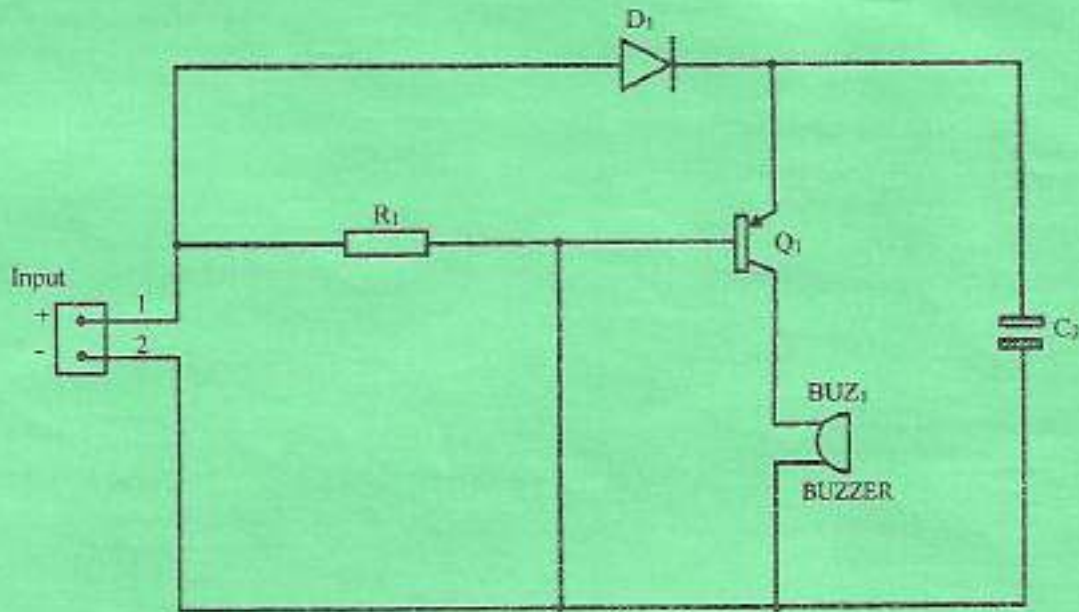


Fig. 6

- (i) Using an appropriate computer software, design the printed circuit board layout (PCB).
- (ii) Print and hand over the hard copy. (10 marks)

(b) Figure 7 shows an electronic circuit.

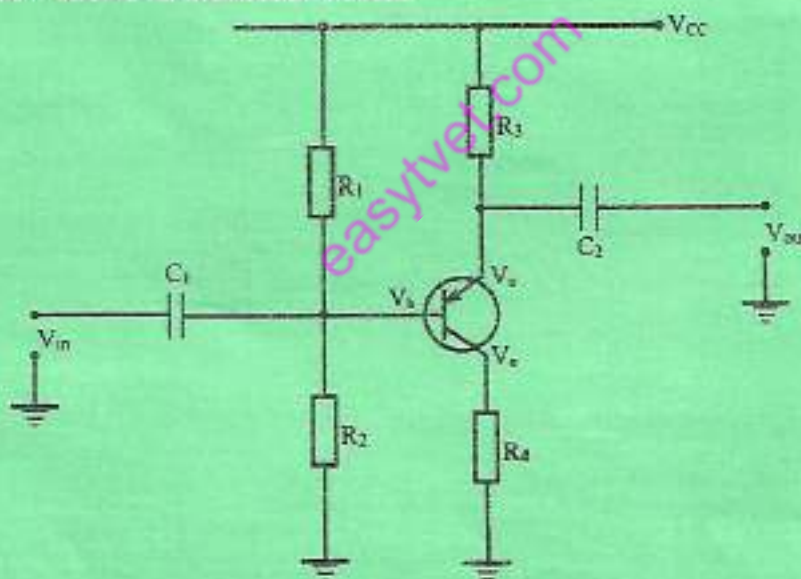


Fig. 7

- (i) Using an appropriate computer software, draw the circuit.
- (ii) Print and hand over the hard copy. (10 marks)

THIS IS THE LAST PRINTED PAGE.