

2521/203 2602/202

2601/202 2603/202

DIGITAL AND ANALOGUE ELECTRONICS II

June/July 2021

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING
(POWER OPTION)
(TELECOMMUNICATION OPTION)
(INSTRUMENTATION OPTION)**

MODULE II

DIGITAL AND ANALOGUE ELECTRONICS II

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Non-programmable scientific calculator;

Drawing instruments.

This paper consists of EIGHT questions in TWO sections; A and B.

Answer TWO questions from section A and THREE questions from section B in the answer booklet provided.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 6 printed pages.

**Candidates should check the question paper to ascertain that
all the pages are printed as indicated and that no questions are missing.**

SECTION A: ANALOGUE ELECTRONICS II

Answer any TWO questions from this section.

1.

- (a) Figure 1 shows an equivalent diagram of a special semi-conductor device.

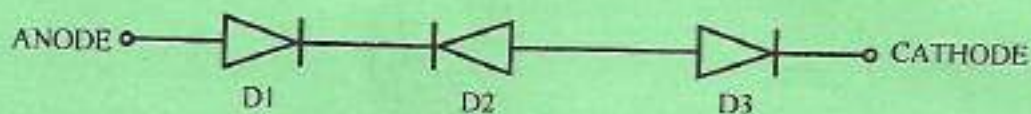


Fig. 1

- (i) Identify the device.
 (ii) Describe its operation. (6 marks)
- (b) (i) State four properties of an ideal operational amplifier (OP-AMP).
 (ii) Define each of the following terms with respect to OP-AMPS:
- I. slew rate;
 - II. common mode rejection ratio. (6 marks)

- (c) Figure 2 shows a multi-stage OP-AMP circuit with an input voltage of $80 \mu\text{V}$.

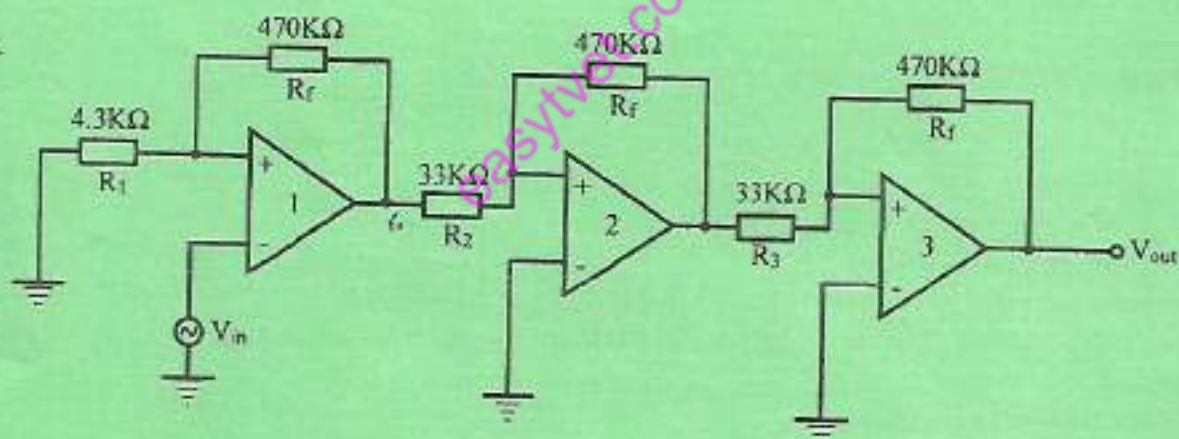


Fig. 2

Determine the:

- (i) voltage gain of the first stage;
- (ii) voltage gain of the second stage;
- (iii) voltage gain of the third stage;
- (iv) overall voltage gain.

(8 marks)

2. (a) Describe each of the following terms as used in transistor oscillators:

- (i) tank circuit;
- (ii) transistor amplifier;
- (iii) feedback circuit.

(6 marks)

(b) (i) State three merits of the Wien Bridge oscillator.

(ii) Figure 3 shows the L-C tank circuit of a Hartley oscillator. The mutual inductance between the two coils is $20 \mu\text{H}$.

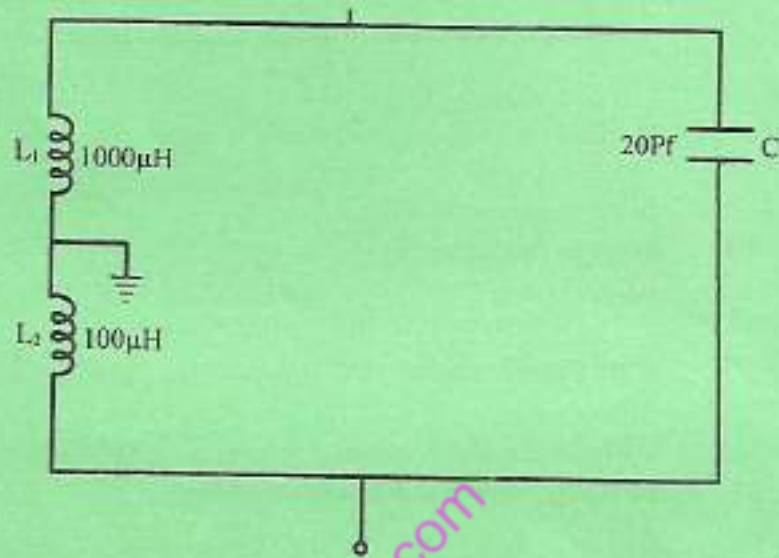


Fig. 3

Determine the:

- I. total inductance;
- II. operating frequency;
- III. feedback fraction.

(9 marks)

(c) With the aid of a labelled circuit diagram, describe the operation of a Triac.

(5 marks)

3. (a) Define each of the following expressions as used in silicon controlled rectifiers (SCRs):

- (i) break over voltage;
- (ii) peak reverse voltage;
- (iii) forward current rating.

(3 marks)

- (b) Figure 4 shows in SCR half-wave rectifier circuit. The SCR has a forward breakdown voltage of 150 V when a current of 1 mA flows in the gate.

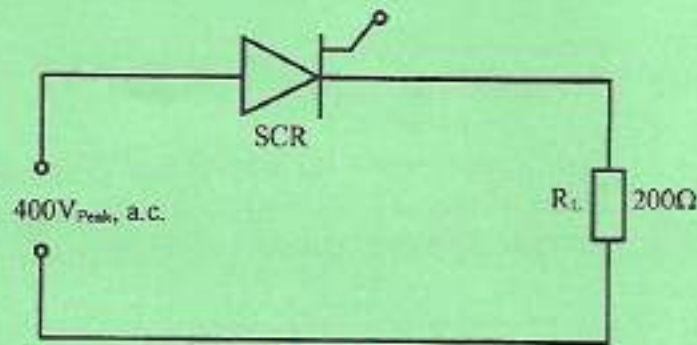


Fig. 4

Determine the:

- (i) firing angle;
 - (ii) average output voltage;
 - (iii) output power. (9 marks)
- (c) (i) State **three** merits of R-C coupled transistor amplifiers.
- (ii) With the aid of a frequency response curve, describe the relationship between gain and frequency for R-C amplifiers. (8 marks)

SECTION B: DIGITAL ELECTRONICS

Answer any **THREE** questions from this section.

- 4 (a) State **three** advantages of digital systems over analogue systems. (3 marks)
- (b) Perform each of the following arithmetic operations:
- (i) $(8C4.37)_{16} + (27B.5D)_{16}$
 - (ii) $(1101101.01)_2 - (1011101.11)_2$
 - (iii) $(1101)_2 \times (1010)_2$ (9 marks)
- (c) Add $(01100100)_2 + (10010010)_2$ in:
- (i) BCD;
 - (ii) X - ccess 3. (6 marks)
- (d) Convert $(110101101)_2$ to Gray code. (2 marks)

2521/203 2602/202

2601/202 2603/202

June/July 2021

5. (a) State De-Morgan's theorems. (2 marks)
- (b) (i) Draw a logic circuit diagram of an S-R flip-flop using NOR gates only.
(ii) Draw the truth table for the flip flop in (b)(i). (7 marks)
- (c) Tables I, II and III show truth tables for different logic gates.

Table I

INPUTS		OUTPUT
A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

Table II

INPUTS		OUTPUT
A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

Table III

INPUTS		OUTPUT
A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

For each truth table:

- (i) Identify the logic gate;
(ii) Draw its symbol;
(iii) Write its Boolean expression. (9 marks)
- (d) Distinguish between Fan-In and Fan-Out as used in logic families. (2 marks)
6. (a) (i) With the aid a schematic block diagrams, describe the operation of a counter based Analogue to Digital Converter (ADC).
(ii) State two merits of the ADC in (a)(i). (9 marks)

(b) A 6-bit successive approximation ADC is used to convert an analogue signal. Determine the:

- (i) percentage resolution;
- (ii) time to convert a half-scale analogue signal, if its clock frequency is $1 \mu\text{Hz}$. (5 marks)

(c) Illustrate implementation of 16-to-1 multiplexer using 4-to-1 multiplexers. (6 marks)

7

(a) Simplify each of the following expressions using Boolean rules:

(i) $Q = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$;

(ii) $Z = \overline{A}\overline{B} + \overline{A}B + A\overline{B}$. (7 marks)

(b) A security alarm system uses four sensors to monitor the four corners of a building. The alarm is triggered when at least two sensors are activated.

- (i) Draw the truth table for the system.
- (ii) Using a K-Map simplify the Boolean expression in (b)(i). (10 marks)

(c) Draw a logic circuit diagram of an OR gate implemented using NAND gates only. (3 marks)

8

(a) Distinguish between volatile and non-volatile memory devices. (2 marks)

(b) A microcomputer has $32 \text{ K} \times 8$ ROM memory. The available memory chips are $8 \text{ K} \times 8$ ROM. Determine the:

- (i) word size;
- (ii) address lines for the entire system;
- (iii) number of chips required for the entire system;
- (iv) draw the system memory map given that the address starts at 0000H . (9 marks)

(c) (i) With the aid of a diagram, describe the operation of a Dynamic RAM memory cell.

(ii) State two merits of the RAM in (c)(i). (9 marks)

THIS IS THE LAST PRINTED PAGE.