

## SECTION A

Answer any **THREE** questions from this section.

1. (a) (i) State Norton's theorem.
- (ii) Figure 1 shows a d.c. circuit. Using Norton's theorem, determine the current flowing in the  $4\Omega$  resistor. Assume the voltage source has negligible internal resistance.

(10 marks)

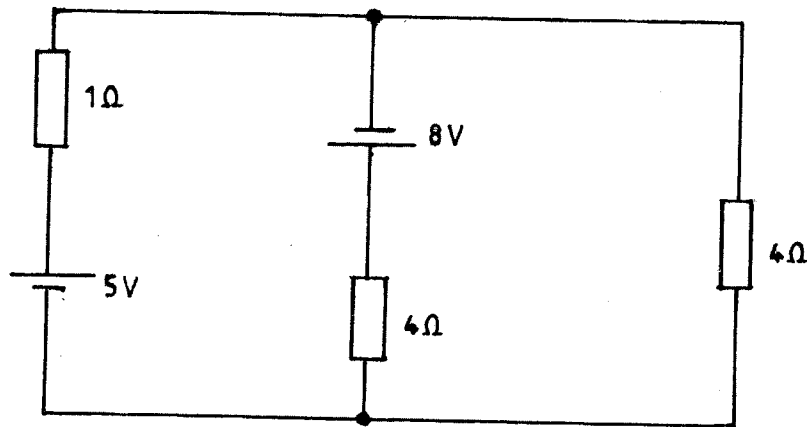


Fig. 1

- (b) Sketch the growth and decay curves for d.c. R-L circuits. (4 marks)
- (c) A d.c. circuit consists of a resistor connected in series with a  $0.5\mu F$  capacitor and has a time constant of 15 ms. Determine the:
- (i) value of the resistor;
- (ii) capacitor voltage 5 ms after connecting the circuit to a 10 V supply. (6 marks)
2. (a) State the functions of the following in a d.c. machine:
- (i) the yoke;
- (ii) pole shoes. (4 marks)
- (b) (i) With the aid of sketches, distinguish between a lap winding and wave winding for d.c. machines.


- (ii) An 8-pole, lap wound d.c. machine has 900 conductors and flux per pole of 0.02 wb. Determine the generated emf when running at a speed of 400 rev/min. (7 marks)
- (c) (i) State **three** applications of stepper motors.
- (ii) With the aid of a labelled diagram, explain the operation of a split phase induction motor. (9 marks)
3. (a) With the aid of diagrams, explain how torque is produced in a three phase induction motor. (9 marks)
- (b) (i) State **three** advantages of wound rotor induction motors as compared with the cage type.
- (ii) A stator winding supplied from a three phase 60 Hz system is required to produce a magnetic flux rotating at 1800 rev/min. Determine its number of poles. (7 marks)
- (c) Explain why a **three** phase synchronous motor is not self starting. (4 marks)
4. (a) (i) With aid of a labelled diagram, explain how three phase E.m.fs are generated.
- (ii) Sketch the waveforms for (a) (i). (7 marks)
- (b) Derive the expression for power in a three star connected balanced loads. (4 marks)
- (c) (i) Draw a Delta-star transformer connected winding and show its terminal markings. (4 marks)
- (ii) A three phase transformer has 200 primary windings and 20 secondary windings. If the supply voltage is 2.2 kV. Determine the secondary line voltage on no-load when the windings are connected in:
- (I) star-delta;
- (II) delta-star. (5 marks)
5. (a) (i) State the **two** components of a complex wave. (2 marks)
- (ii) Differentiate between odd and even harmonics. (4 marks)

- (iii) A complex voltage is given by  
 $e = 140 \sin wt + 40 \sin 3wt$   
The corresponding current in the load is given by  
 $i = 10 \sin (wt + 60^\circ) + 8 \sin (3wt - 30^\circ)$ .  
Determine the total power supplied. (4 marks)
- (b) (i) State **two** most important properties of two port network. (2 marks)
- (ii) Sketch the characteristic impedance/frequency characteristics of a T constant-K low pass filter. (2 marks)
- (c) A constant  $K$  low pass filter using a  $\pi$  section has a design impedance of  $0.4K\Omega$  and a cut-off frequency of 2 kHz. Determine the component values for the filter. (6 marks)

**SECTION B**

Answer any **TWO** questions from this section.

6. Figure 2 shows three views of an object drawn in third angle projection. Copy the views using AutoCAD and insert **six** major dimensions. Draw the symbol of third angle projection. Print your work and attach it with your other completed drawings. (20 marks)

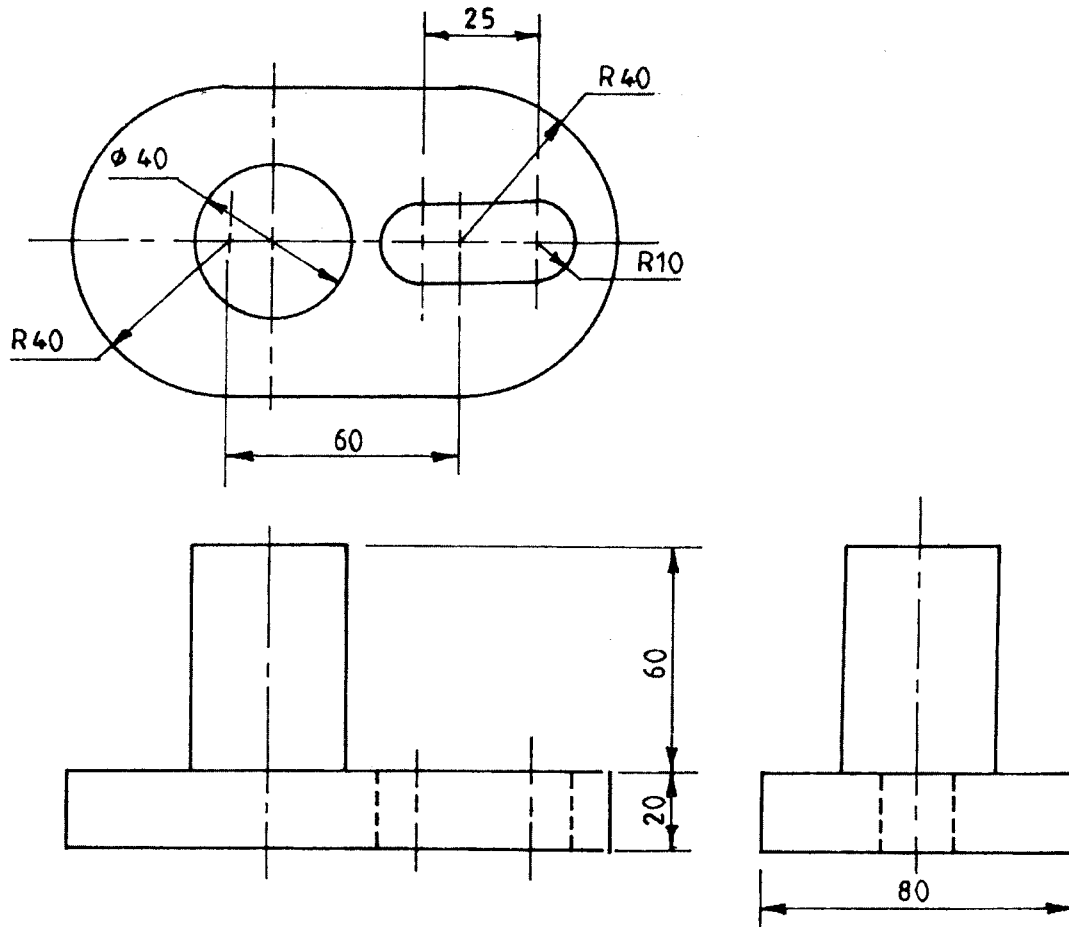

**Fig. 2**

7. (a) Sketch the following BS 3939 electrical and electronic symbols:

- (i) Switched socket outlet;
- (ii) One way switch;
- (iii) Cooker unit;
- (iv) Energy meter;
- (v) Isolator;
- (vi) Battery;
- (vii) Inductor;
- (viii) NOR gate;
- (ix) Potentiometer;
- (x) AND-gate.

(10 marks)

(b) Draw the transistor amplifier circuits connected in the following configurations:

- (i) common-emitter;
- (ii) common-collector.

(10 marks)

8. Draw separately, the control and power circuit diagrams for automatic star-delta starting for a three phase induction motor with time delay. (20 marks)

**THIS IS THE LAST PRINTED PAGE.**